



DIGITAL DESIGN

ASSIGNMENTREPORT


ASSIGNMENT ID : 03

Student Name: Weibao Fu


Student ID: 11812202

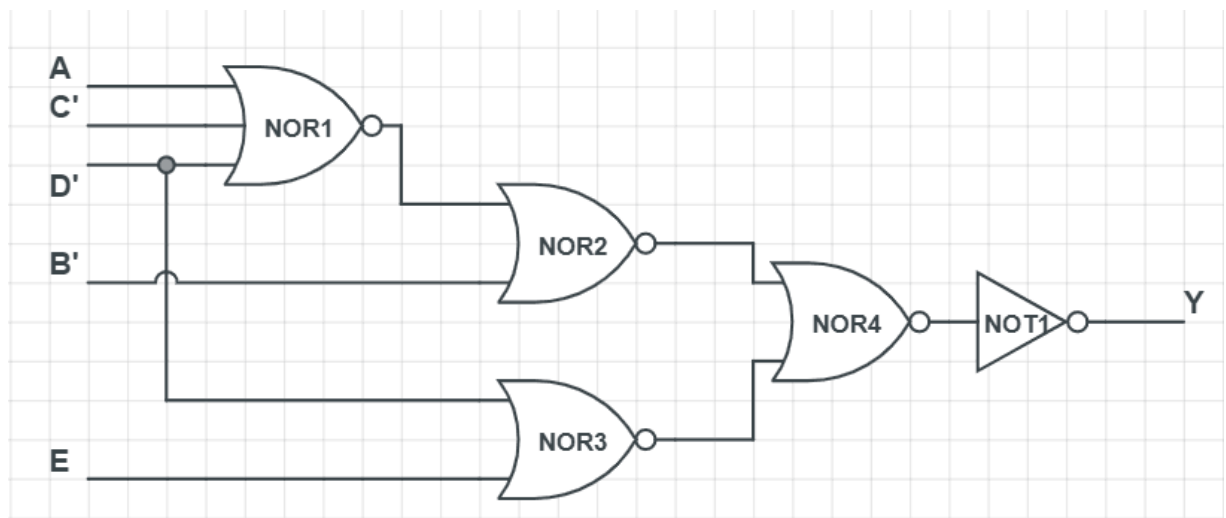PART 1: DIGITAL DESIGN THEORY

$$\begin{aligned}
 1. \quad Y &= AB(D + C) + (BC' + DE') + BD' \\
 &= ABD + ABC + BC' + DE' + BD' \\
 &= AB + BC' + BD' + DE' \\
 &= B(A + C' + D') + (D' + E)' \\
 &= (B' + (A + C' + D'))' + (D' + E)' \\
 &= ((B' + (A + C' + D'))' + (D' + E))'
 \end{aligned}$$



 2. From the Boolean Function, we can get this Karnaugh maps.



We can get the simple function of F is $F = AB' + AD + C'D + A'BC'$

$$(a) F = AB' + AD + C'D + A'BC'$$

$$= AB' + AD + C'D + ((A'B)' + C)'$$

$$= (((AB' + AD) + C'D) + ((A'B)' + C)')$$

$$(b) F = AB' + AD + C'D + A'BC'$$

$$= (A' + B)' + (A' + D)' + (C + D')' + (A + B' + C)'$$

$$= ((A' + B) (A' + D'))' + (C + D')' + ((A + B')'C')''$$

$$= ((A' + B) (A' + D'))' + ((C + D') ((A + B')'C'))'$$

$$= (((A' + B) (A' + D'))'' ((C + D') ((A + B')'C'))'')'$$

$$(c) F = AB' + AD + C'D + A'BC'$$

$$= (A' + B)' + (A' + D)' + (C + D')' + (A + B' + C)'$$

$$= ((A' + B)' + (A' + D'))'' + ((C + D')' + ((A + B')'' + C))''$$

$$(d) F = AB' + AD + C'D + A'BC'$$

$$= ((AB')'(AD)')(C'D)'(A'BC')'$$

$$= (((AB')'(AD))''((C'D)'((A'B)''C'))'')'$$

$$(e) F = AB' + AD + C'D + A'BC'$$

$$= (A + C')(A' + B' + D)(B' + C' + D)(A + B + D)$$

$$= ((A + C')((A' + B') + D))(((B' + C') + D)((A + B) + D))$$

$$(f) F' = \sum(0, 2, 3, 6, 7, 12, 14)$$

$$= A'C + ABD' + A'B'D'$$

$$F = (F')' = (((A+C')' + ((A' + B')'' + D))'' + ((A + B)'' + D)')'$$

$$(g) F = AB' + AD + C'D + A'BC'$$

$$= ((AB')'(AD)')(C'D)'(A'BC')'$$

$$= (((AB')'(AD))''(C'D)'(((A'B)''C'))'')'$$

3.

Four-bit parity generator

*Truth table

A	B	C	D	Y(odd)	Y(even)
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	0	1
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	0	1
1	1	0	0	1	0
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	0


$$*Y(\text{odd})=A'B'C'D'+A'B'CD+A'BC'D+AB'C'D + A'BCD' + AB'CD' + ABC'D' + ABCD$$

$$= (A \oplus B \oplus C \oplus D)'$$

$$Y(\text{even})=A'B'C'D+A'B'CD'+A'BC'D'+AB'C'D'+ A'BCD + AB'CD + ABC'D + ABCD'$$

$$= A \oplus B \oplus C \oplus D$$

*The circuit diagram

 

Three-bit parity checker

Four-bit parity generator

*Truth table


A	B	C	O	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0

1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$*Y=A'B'C'O+A'B'CO'+A'BC'O'+AB'C'O'+A'BCO+AB'CO+ABC'O+ABCO'$$

$$= A \oplus B \oplus C \oplus O$$

Circuit diagram

 

4. From the given problem, we can get the truth table.


x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

Such that, we can get $A(x, y, z) = yz' + xz$

$$B(x, y, z) = x'y' + y \odot z$$

$$C(x, y, z) = xz' + x'y'z$$

Circuit diagram

 

5.(Here we assume that the 7-seg tube is high level active)

Truth table

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1

0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Such that $a(A, B, C, D) = \sum(0,2,3,5,6,7,8,9) = A'C + B'C'D' + A'BD + AB'C'$

$b(A, B, C, D) = \sum(0,1,2,3,4,7,8,9) = A'CD + A'C'D' + A'B' + B'C'$

$c(A, B, C, D) = \sum(0,1,3,4,5,6,7,8,9) = A'B + A'C' + A'D + B'C'$


$d(A, B, C, D) = \sum(0,2,3,5,6,8,9)$

$= A'B'C + A'B'D' + A'BC'D + A'CD' + AB'C'$

$e(A, B, C, D) = \sum(0,2,6,8) = A'CD' + B'C'D'$

$f(A, B, C, D) = \sum(0,4,5,6,8,9) = AB'C' + A'BC' + A'BD' + A'C'D'$

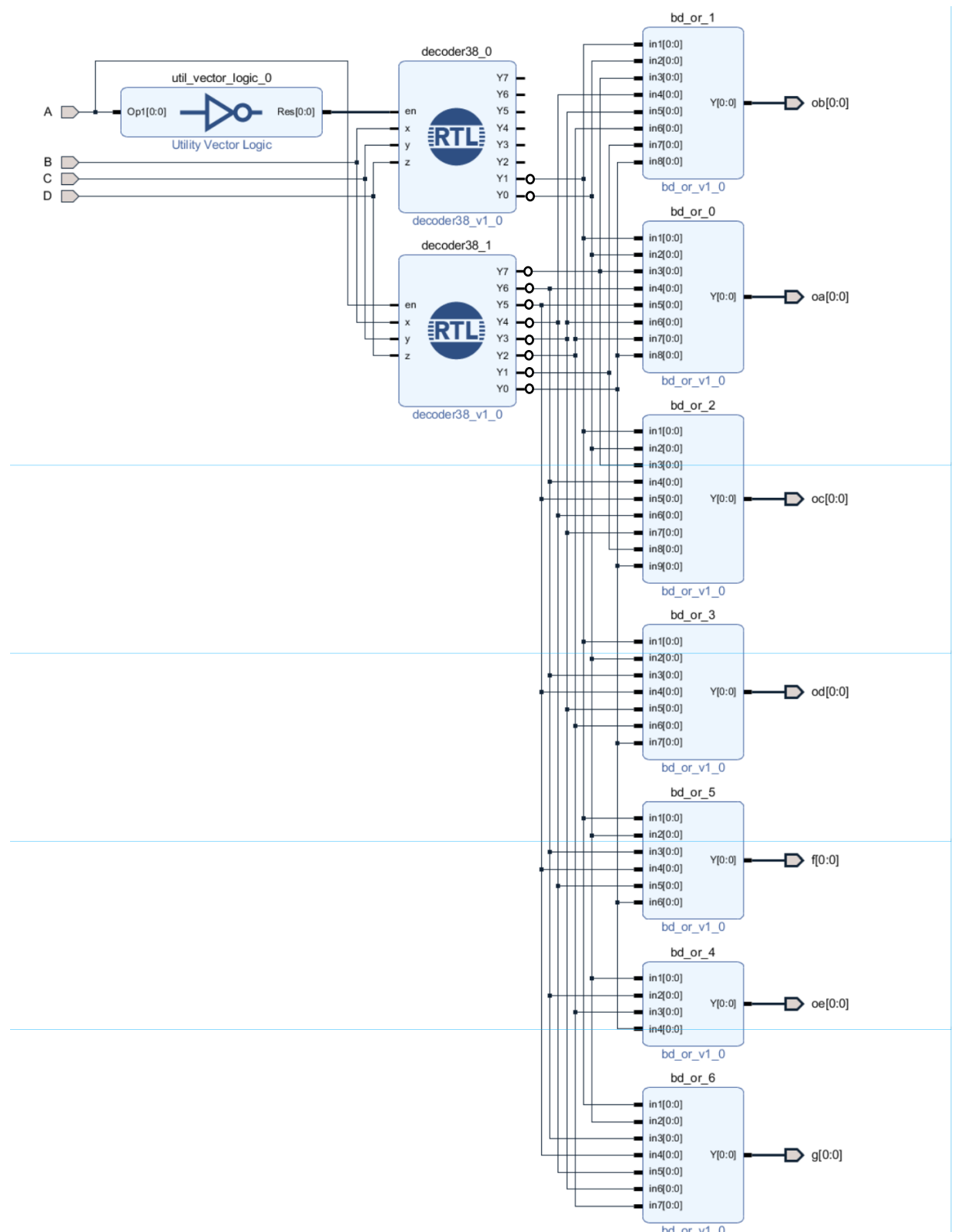$g(A, B, C, D) = \sum(2,3,4,5,6,8,9) = AB'C' + A'BC' + A'B'C + A'CD'$



6. Assume the unsigned number are $A_4A_3A_2A_1$, $B_4B_3B_2B_1$.

Then we can get

$$\begin{array}{r} A_4 \ A_3 \ A_2 \ A_1 \\ \times \ B_4 \ B_3 \ B_2 \ B_1 \\ \hline \end{array}$$

We set C_{in} as carry. From this, if


we multiple B_i with $A_4A_3A_2A_1$ one by one, and we add the result, then we set the highest as C_{in} , and participate the next adder. As a result, we can get the answer.

The logic formula is that:

Assume $\text{Adder}(abcd, edfg) = rmnpq$, such that $C_i = q$ and $C_{in} = r$.

Then the next step is $\text{Add}(a'b'c'd', rd'f'g')$.

The circuit diagram:

 


7. (a) Since $F(A, B, C, D) = \sum (0, 2, 5, 8, 10, 14)$

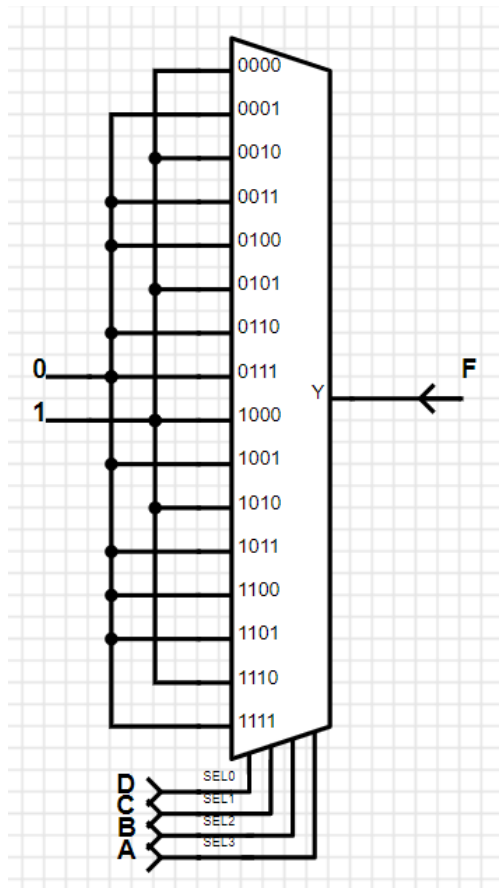
(b) Since $F(A, B, C, D) = \prod (2, 6, 11)$

$$= \sum (0, 1, 3, 4, 5, 7, 8, 9, 10, 12, 13, 14, 15)$$

We can implement the Boolean function as below.



(a)

 

(b)

8. Assume A is subtrahend, B is minuend, C is a bit that borrow from the lower position, D is the result, E is a bit that borrow from the higher position.

Truth table:

A	B	C	D	E
0	0	0	0	0
0	0	1	1	1

0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Such that, $D(A, B, C) = \sum(1, 2, 4, 7)$ $E(A, B, C) = \sum(1, 2, 3, 7)$


Since $D = D_{10}A_1'A_0' + D_{11}A_1'A_0 + D_{12}A_1A_0' + D_{13}A_1A_0$

LET $A_1 = B, A_0 = C$, THEN $D_{10}=D_{13}=A, D_{11}=D_{12}=A'$

Since $E = D_{20}A_1'A_0' + D_{21}A_1'A_0 + D_{22}A_1A_0' + D_{23}A_1A_0$

LET $A_1 = B, A_0 = C$, THEN $D_{20}=0, D_{21}=D_{22}=A', D_{23}=1$

Circuit diagram:

 

9. Since $F = I_0D_0 + I_1D_1 + I_2D_2 + I_3D_3 + I_4D_4 + I_5D_5 + I_6D_6 + I_7D_7$

$$= C'B'A' + DC'B'A + C'BA' + D'C'BA + D'CB'A + DCBA'$$

$$= (D+D')C'B'A'+DC'B'A+(D+D')C'BA'+D'C'BA+D'CB'A+DCBA'$$

$$F(A, B, C, D) = \sum(0,1,4,5,7,9,10,12)$$

PART 2: DIGITAL DESIGN LAB (TASK1)

DESIGN

Multiplexer

**Design Verilog Code*

```
`timescale 1ns / 1ps

module Multiplexer74151(EN,S1,S0,D3,D2,D1,D0,Y);
input EN,S1,S0,D3,D2,D1,D0;
output reg Y;
always @*
if(~EN)
    case({S1,S0})
        2'b00: Y=D0;
        2'b01: Y=D1
        2'b10: Y=D2;
        2'b11: Y=D3;
    endcase
else
    Y=1'b0;
endmodule
```

**Simulation Verilog Code*

```
`timescale 1ns / 1ps

module sim_1();
reg EN,S1,S0,D3,D2,D1,D0;
wire Y;
```

```
Multiplexer74151 usim(EN,S1,S0,D3,D2,D1,D0,Y);
```

```
initial
```

```
begin
```

```
{EN,S1,S0,D3,D2,D1,D0} = 7'b0000000;
```

```
while({EN,S1,S0,D3,D2,D1,D0}<7'b1111111)
```

```
begin
```

```
#10 {EN,S1,S0,D3,D2,D1,D0} = {EN,S1,S0,D3,D2,D1,D0}+1;
```


```
end
```

```
#10 $finish(1);
```

```
end
```

```
endmodule
```

*Wave Form

 

From the wave form, we can get:

When 0-160ns: EN=0, and {S1,S0}=2'b00, such that the wave of Y is same as D0.

When 170-320ns: EN=0, and {S1,S0}=2'b01, such that the wave of Y is same as D1.

When 330-480ns: EN=0, and {S1,S0}=2'b10, such that the wave of Y is same as D2.

When 490-640ns: EN=0, and {S1,S0}=2'b11, such that the wave of Y is same as D3.

When 650-1280ns: EN=1, such that Y=0;

Full subtractor

Assume A is subtrahend, B is minuend, C is a bit that borrow from the lower position, D is the result, E is a bit that borrow from the higher position.

*Truth table:

A	B	C	D	E
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

**Design Verilog Code*

```
`timescale 1ns / 1ps
module Sub(A,B,C,D,E);
input A,B,C;
output D,E;
wire zero = 0 ;
wire one = 1;
Multiplexer74151 mult1(zero,B,C,A,~A,~A,A,D);
Multiplexer74151 mult2(zero,B,C,one,~A,~A,zero,E);
endmodule
```

SIMULATION

Simulation Verilog Code

```
`timescale 1ns / 1ps

module sim_sub( );

reg A,B,C;


wire D,E;

Sub usim(A,B,C,D,E);

initial
begin
    {A,B,C} = 3'b000;
    while({A,B,C}<3'b111)
    begin
        #10 {A,B,C}={A,B,C}+1;
    end
    #10 $finish();
end

endmodule
```

Wave Form

 

From the Wave Form, we can get:

When 0-10ns, {A,B,C}=3'b000, then D=0, E=0;

When 10-20ns, {A,B,C}=3'b001, then D=1, E=1;

When 20-30ns, {A,B,C}=3'b010, then D=1, E=1;

When 30-40ns, {A,B,C}=3'b011, then D=0, E=1;

When 40-50ns, {A,B,C}=3'b100, then D=1, E=0;

When 50-60ns, {A,B,C}=3'b101, then D=0, E=0;

When 60-70ns, {A,B,C}=3'b110, then D=0, E=0;


When 70-80ns, {A,B,C}=3'b111, then D=1, E=1;

CONSTRAINT FILE AND THE TESTING

Constraint File

```
set_property PACKAGE_PIN Y9 [get_ports A]
set_property IOSTANDARD LVCMOS33 [get_ports A]
set_property PACKAGE_PIN Y7 [get_ports C]
set_property PACKAGE_PIN W9 [get_ports B]
set_property IOSTANDARD LVCMOS33 [get_ports B]
set_property PACKAGE_PIN K17 [get_ports D]
set_property PACKAGE_PIN L13 [get_ports E]
set_property IOSTANDARD LVCMOS33 [get_ports D]
set_property IOSTANDARD LVCMOS33 [get_ports E]
set_property IOSTANDARD LVCMOS33 [get_ports C]
```

Analysis

 


Testcase #1

When input is 0 - 0,

And it borrow from lower position is 0

 Then the output is 0, the borrow from higher position is 0




Testcase #2

When input is 0 - 0,

And it borrow from lower position is 1

 Then the output is 1, the borrow from higher position is 1




Testcase #3

When input is 0 - 1,

And it borrow from lower position is 0

 Then the output is 1, the borrow from higher position is 1




Testcase #4

When input is 0 - 1,

And it borrow from lower position is 1

 Then the output is 0, the borrow from higher position is 1




Testcase #5

When input is 1 - 0,

And it borrow from lower position is 0

 Then the output is 1, the borrow from higher position is 0




Testcase #6

When input is 1 - 0,

And it borrow from lower position is 1

 Then the output is 0, the borrow from higher position is 0




Testcase #7

When input is 1 - 1,

And it borrow from lower position is 0

 Then the output is 0, the borrow from higher position is 0



Testcase #8

When input is 1 - 1,

And it borrow from lower position is 1

Then the output is 1, the borrow from higher position is 1

THE DESCRIPTION OF OPERATION

No Problem

PART 2: DIGITAL DESIGN LAB (TASK2)

DESIGN

3-8 Decoder

*Verilog Code

```
`timescale 1ns / 1ps

module decoder38(en,x,y,z,Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0);
input en,x,y,z;
output reg Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0;
always @*
begin
    if(~en)
        case({x,y,z})
            3'b000: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b00000001;
            3'b001: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b00000010;
```

```

3'b010: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b00000100;
3'b011: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b00001000;
3'b100: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b00010000;
3'b101: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b00100000;
3'b110: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b01000000;
3'b111: {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b10000000;

endcase

else {Y7,Y6,Y5,Y4,Y3,Y2,Y1,Y0} = 8'b00000000;

end

endmodule


```

**Truth table (The 7-seg tube is low active)*

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	0	0	1	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	0	1	0	0
0	1	1	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	1	0	0
1	0	1	0	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	1	1	1

1	1	1	0	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1

ABCD-to-7 segment

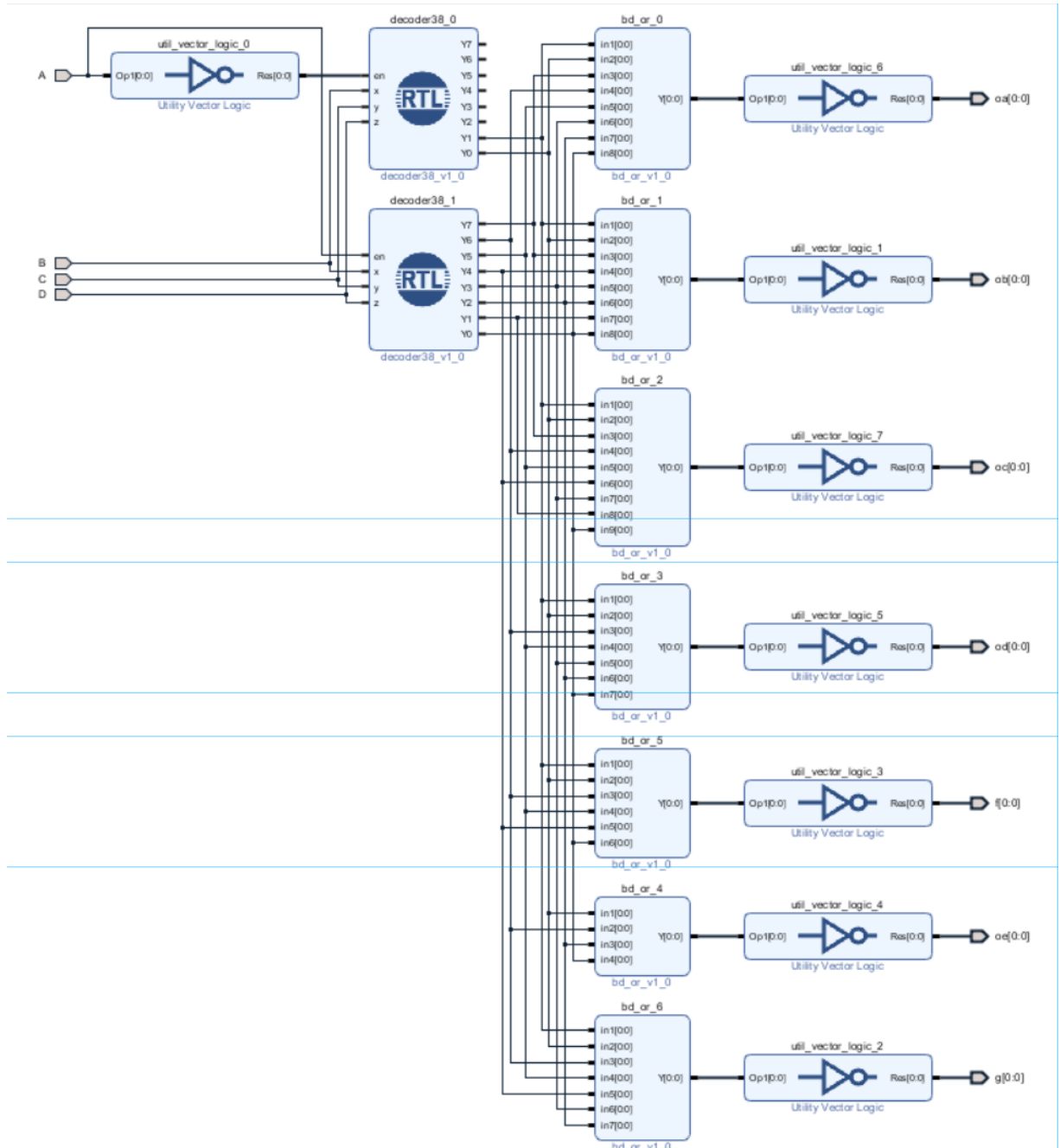

*Design Verilog Code

```

`timescale 1 ps / 1 ps

module ABCD_seg_wrapper(A,B,C,D,f,g,oa,ob,oc,od,oe);

    input wire A,B,C,D;

    output wire f,g,oa,ob,oc,od,oe;

    ABCD_seg ABCD_seg_i(.A(A),.B(B),.C(C),.D(D),.f(f),.g(g),
.oa(oa),.ob(ob),.oc(oc),.od(od),.oe(oe));

endmodule

```

SIMULATION

Simulation Verilog Code

```

`timescale 1ns / 1ps

module sim_u( );

    reg A,B,C,D;

    wire a,b,c,d,e,f,g;

    ABCD_seg_wrapper u(A,B,C,D,f,g,a,b,c,d,e);

    initial
    begin
        {A,B,C,D}=4'b0000;

        while({A,B,C,D}<4'b1111)

        begin

            #10 {A,B,C,D}={A,B,C,D}+1;

        end


        #10 $finish();

    end

endmodule

```

Wave Form

 

From the Wave Form

0-10ns, $\{A,B,C,D\}=0000$, $\{a,b,c,d,e,f,g\}=0000001$, which display 0 in 7-seg tube

10-20ns, $\{A,B,C,D\}=0001$, $\{a,b,c,d,e,f,g\}=1001111$, which display 1 in 7-seg tube;

20-30ns, $\{A,B,C,D\}=0010$, $\{a,b,c,d,e,f,g\}=0010010$, which display 2 in 7-seg tube;

30-40ns, $\{A,B,C,D\}=0011$, $\{a,b,c,d,e,f,g\}=0000110$, which display 3 in 7-seg tube;

40-50ns, $\{A,B,C,D\}=0100$, $\{a,b,c,d,e,f,g\}=1001100$, which display 4 in 7-seg tube;

50-60ns, $\{A,B,C,D\}=0101$, $\{a,b,c,d,e,f,g\}=0100100$, which display 5 in 7-seg tube;

60-70ns, $\{A,B,C,D\}=0110$, $\{a,b,c,d,e,f,g\}=0100000$, which display 6 in 7-seg tube;

70-80ns, $\{A,B,C,D\}=0111$, $\{a,b,c,d,e,f,g\}=0001111$, which display 7 in 7-seg tube;

80-90ns, $\{A,B,C,D\}=1000$, $\{a,b,c,d,e,f,g\}=00000000$, which display 8 in 7-seg tube;

90-100ns, $\{A,B,C,D\}=1001$, $\{a,b,c,d,e,f,g\}=0000100$, which display 9 in 7-seg tube;

100-160ns, $\{a,b,c,d,e,f,g\} = 1111111$, which display nothing in 7-seg tube.

CONSTRAINT FILE AND THE TESTING

Constraint File

```
set_property IOSTANDARD LVCMOS33 [get_ports {0a}]
set_property IOSTANDARD LVCMOS33 [get_ports {0b}]
set_property IOSTANDARD LVCMOS33 [get_ports {0c}]
set_property IOSTANDARD LVCMOS33 [get_ports {0d}]
set_property IOSTANDARD LVCMOS33 [get_ports {0e}]
set_property IOSTANDARD LVCMOS33 [get_ports {f}]
set_property IOSTANDARD LVCMOS33 [get_ports {g}]
set_property IOSTANDARD LVCMOS33 [get_ports {A}]
set_property IOSTANDARD LVCMOS33 [get_ports {B}]
set_property IOSTANDARD LVCMOS33 [get_ports {C}]
set_property IOSTANDARD LVCMOS33 [get_ports {D}]
set_property PACKAGE_PIN C15 [get_ports {g}]
set_property PACKAGE_PIN C14 [get_ports {f}]
set_property PACKAGE_PIN E17 [get_ports {0e}]
set_property PACKAGE_PIN F16 [get_ports {0d}]
set_property PACKAGE_PIN F14 [get_ports {0c}]
set_property PACKAGE_PIN F13 [get_ports {0b}]
set_property PACKAGE_PIN F15 [get_ports {0a}]
set_property PACKAGE_PIN Y9 [get_ports {A}]
set_property PACKAGE_PIN W9 [get_ports {B}]
set_property PACKAGE_PIN Y7 [get_ports {C}]
set_property PACKAGE_PIN Y8 [get_ports {D}]
```


Analysis



Testcase #1

When input is 0000,


It will display 0

 

Testcase #2

When input is 0001,

It will display 1

 

Testcase #3

When input is 0010,

It will display 2



Testcase #4

When input is 0011,

It will display 3



Testcase #5

When input is 0100,

It will display 4



Testcase #6

When input is 0101,

It will display 5



Testcase #7

When input is 0110,

It will display 6



Testcase #8

When input is 0111,

It will display 7



Testcase #9

When input is 1000,

It will display 8



Testcase #10

When input is 1001,

It will display 9



Testcase #11

When input is 1010,

It will display nothing



Testcase #12

When input is 1111,

It will display nothing

THE DESCRIPTION OF OPERATION

No Problem